



1.12 eV

*keep it static  
dependant and temperature  
is what matters!*

# CMOS GATES

$pmos = \downarrow$

James E. Stine, Jr.

Edward Joullian Endowed Chair in Engineering

Oklahoma State University

Electrical and Computer Engineering Department

Stillwater, OK 74078 USA

[james.stine@okstate.edu](mailto:james.stine@okstate.edu)





[Wiki]

# Layers

- To tell equipment where to dope materials, layers were introduced into software tools to give them order.
  - Much of these tools are software categorized into an area called Electronic Design Automation software and can include the Printed Circuit Board area, as well.
- Each color is usually represented by a different layer and possibly number or keyword.
  - Some colors may also have a “stipple” pattern as well (i.e., shading using dots).
  - Historically, some colors have sentimental feelings for people and, thus, are passed down in terms of the representation (e.g, metal1 or 1<sup>st</sup> layer metal is typically blue) and other colors are random by tool.
- Multiple layers can possibly overlap with each other, but it is the job of the technology file to indicate where there are errors.
  - Sometimes this is called Design Rule Checking (DRC).
  - Most layers have spacing and length rules.
- Certain layers may be grouped together to create a structure, such as a transistor.

# Simple Model of a MOSFET


Three  
Terminal  
Device

  

- Source or Drain : depends entirely on the bias.
  - Two ends of the conductive path.
- Gate
  - Controls conductive path.
- Operation
  - Conducts when gate is high
  - Open circuit when gate is low
  - Reality Check: passes zero great, but not ones.

# Switch Networks

---

 

Abstract Switch.


- Since transistors can be modeled as simple switches.
  - Utilize an abstract switch where top is a valve which allows the ports to connect
  - Define a function of a switch network as the input conditions that connect the two terminals of the network  $port\_out = port\_in \text{ valve}$
- Structure of switch networks defines its logic function:
  - OR functions are constructed by parallel switches.
  - AND functions are constructed by series switches.

*Do NMOS first!*
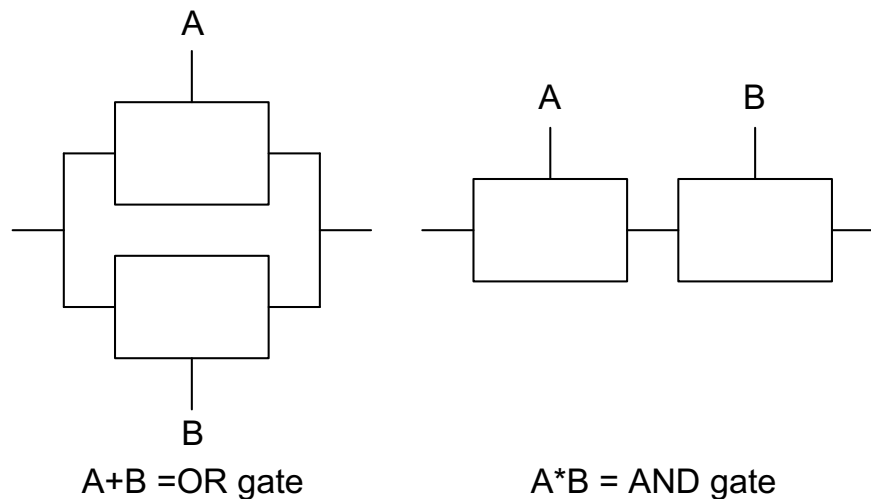
# The Switch Networks

---

- The function of a switch is true when the input terminals of the network are connected together.
  - For parallel switches: if either function is on, the function is an OR
  - For series switches: if both functions are on, the function is an AND




Abstract Switch
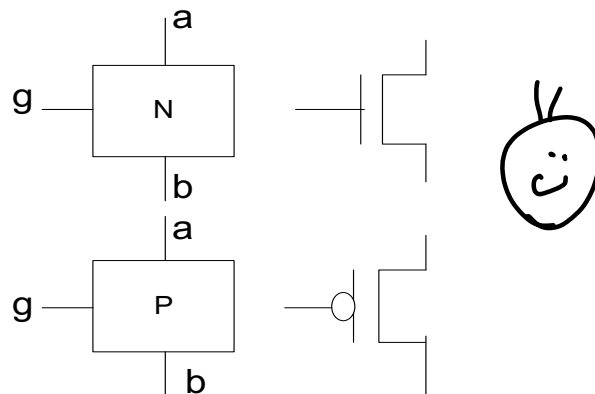
# The Switch Model

---

- The simplest model of a MOS transistor is a simple 3-terminal switch!
- n-switch:  $g=1$  closes the switch
- n-switch: passes 1's poorly, good 0's
- p-switch:  $g=0$  closes the switch
- p-switch: passes 0's poorly, good 1's




# Switches and more Switches

---

- More complex switches are possible.
- Composition rules are simple.
  - Parallel combinations of switches yields an OR of the component switch networks' function.
  - Series combinations of switches yields an AND of the component switch networks' function.

# What function am I?

 

Unknown Function???




# Rules for Switches

---

- Using switch networks, we can build up a simple kind of logic. The basic idea is to use switches to route one or more inputs to the output.
- There are two rules you must follow for switch logic to work.
  - The primary output must always be connected to one of the inputs
    - That is, the OR of all the switch-networks to the output must be 1.
  - Two or more inputs must not be connected together
    - That is, the AND of any two of the switch-networks to the output must be 0 unless they are both constants and have the same value.

 
# Transistors as Switches

- We can view MOS transistors as electrically controlled switches
- Voltage at gate controls path from source to drain


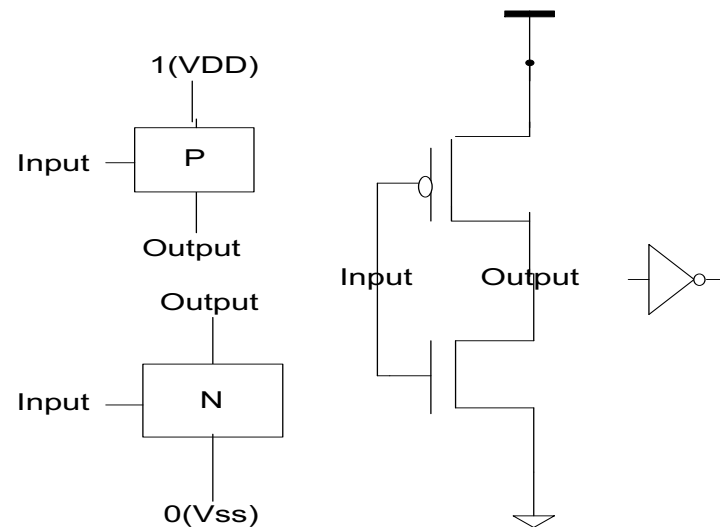
# Logic Inversion

- To achieve any function easily, it would be advantageous to create an inverted signal.
  - That is, the ability to change a signal's digital level from a 1 to a 0 and vice-versa.
  - An inverter can be built using two (n and p) MOS transistors.





Inverter

# CMOS Inverter

---


A	Y
0	
1	0

  

# CMOS Logic

## Example 1

	Input A	Input B	Gate		
Case	(NMOS)	(NMOS)	1	2	Output
1	0	0	Off	Off	0
2	0	1	Off	On	0
3	1	0	On	Off	0
4	1	1	On	On	1

 

# CMOS Logic

## Example 2

	Input A	Input B	Gate		
Case	(PMOS)	(PMOS)	1	2	Output
1	0	0	On	On	1
2	0	1	On	Off	0
3	1	0	Off	Off	0
4	1	1	Off	Off	0

Series PMOS.




# CMOS Logic

## Example 3

	Input A	Input B	Gate		
Case	(NMOS)	(NMOS)	1	2	Output
1	0	0	Off	Off	0
2	0	1	Off	On	1
3	1	0	On	Off	1
4	1	1	On	On	1

Parallel NMOS

 

# CMOS Logic

---

## Example 4

	Input A	Input B	Gate		
Case	(PMOS)	(PMOS)	1	2	Output
1	0	0	On	On	1
2	0	1	On	Off	1
3	1	0	Off	On	1
4	1	1	Off	Off	0

Parallel PMOS.



# Logic Gates

---

The general structure of a complex logic gate can be created by the following steps:

- Provide a complementary pair (nMOS and pMOS with a common gate) for each input.
- Replace the nMOS with an array of nMOSs that connect the output to ground (VSS).
- Replace the pMOS with an array of pMOS gates that connect the output to VDD.
  - That is, the ability to change a signals digital level from a 1 to a 0 and vice-versa.
    - An inverter can be built using two (n and p) MOS transistors.

# Operation of the CMOS Inverter Circuit


*Perfect load*

---

- Voltage  $V_{in}$  controls the conduction modes of both transistors.
- When  $V_{in} = V_{DD}$ , the nMOS is ON and transmits the ground (Logic 0).
- When  $V_{in} = V_{SS}$ , the pMOS is ON and transmits the power supply voltage ( $V_{DD}$ ) to the output (Logic 1).
- The search for the perfect load is over!!!

# Operation of the CMOS Inverter Circuit

---

 


$$\sum_{k=1}^n V_k = 0$$

# The CMOS NAND Gate

---

Input A	Input B	Output
0	0	1
0	1	1
1	0	1
1	1	0

Table 5: Truth Table for Logic NAND.

 


# The CMOS NAND Gate

---

- Want to have complementary pair that act in tandem.
- When one is on, you want the other off
- Connect two N-transistors in series from output to VSS
- Connect two P-transistors in parallel from output to VDD

# The CMOS NAND Gate

---

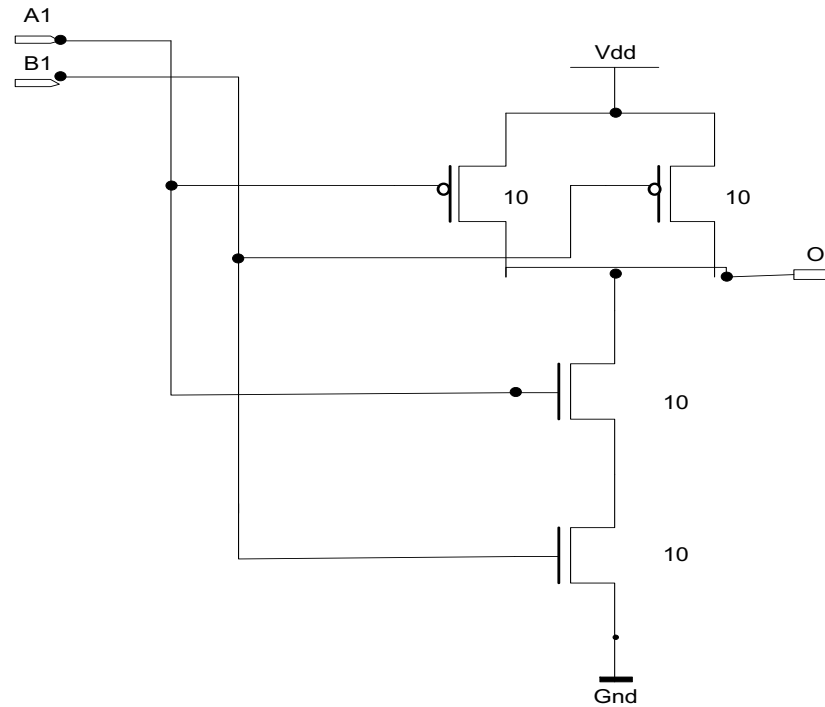

NAND Gate

# The CMOS NAND Gate

---

Input A1	Input B1	Output
0 V	0 V	VDD
0 V	5 V	VDD
5 V	0 V	VDD
5 V	5 V	VSS

Parallel PMOS

$$f = (\overline{A1} + \overline{B1}) \cdot 1 + (A1 \cdot B1) \cdot 0$$

$$f = (\overline{A1} + \overline{B1})$$


$$f = \overline{(A1 \cdot B1)}$$

# The CMOS NOR Gate

---

Input A	Input B	Output
0	0	1
0	1	1
1	0	1
1	1	0

Truth Table for Logic Nor.

 




# The CMOS NOR Gate

---

- Want to have complementary pair that act in tandem.
- When one is on, you want the other off
- Connect two N-transistors in parallel from output to VSS
- Connect two P-transistors in series from output to VDD

# The CMOS NAND Gate

---

 

NOR Gate

# The CMOS NAND Gate

---

Input A1	Input B1	Output
0 V	0 V	VDD
0 V	5 V	VSS
5 V	0 V	VSS
5 V	5 V	VSS

Parallel NMOS

$$f = (\overline{A1} \cdot \overline{B1}) \cdot 1 + (A1 \cdot B1) \cdot 0$$

$$f = \overline{(\overline{A1} \cdot \overline{B1})}$$

$$f = \overline{(A1 + B1)}$$


# The Static CMOS Gate

---

- As you can see each gate will have complementary pair.
- In addition, you can see they always act in tandem.
- Since the top part of the circuit (the PMOS) act by pulling the logic level up they are called *Pullup devices* which is abbreviated as **PUN**  
*Pull up network*
- Since the bottom part of the circuit (the NMOS) act by pulling the logic level down they are called *Pulldown devices* which is abbreviated as **PDN**  
*Pull down network*

 
# Symbols

- So far, we have treated transistors as ideal switches
- An ON transistor passes a finite amount of current
  - Depends on terminal voltages
  - Derive current-voltage (I-V) relationships
- Transistor gate, source, drain all have capacitance
  - Capacitance and current determine speed


 
# Transistors as Switches

- We can view MOS transistors as electrically controlled switches
- Voltage at gate controls path from source to drain



# Summary

---

- CMOS gates are easy to create for most inverting-type logic.
- They also produce a very "clean" VTC which is great for digital systems.
- Resiliency is also key for CMOS as they are great at switching for systems.
- There is an equal number of pMOS and nMOS transistors in a system for most gates.
- Most CMOS gates tend to use around 4 as the maximum number of inputs to a digital gate.
  - This is changing for different technologies and lower feature sizes.